

Report on Hardware project

AI1110: Probability and Random Variables
Indian Institute of Technology Hyderabad

Bolla Nehasree
CS22BTECH11012

Experiment Report:

Generating Random Numbers using digital logic components.

Components:

- Breadboard
- Seven Segment (Common Anode) Display
- Decoder (7447)
- 2 Flip Flops (7474)
- X-OR Gate (7486)
- 555 IC
- Resistor (1K Ω)
- Resistor (1M Ω)
- Capacitor (100nF)
- Capacitor (10nF)
- Connecting Wires
- Micro USB

Description:

The breadboard provides a platform for easily connecting electronic circuits without the need for soldering. First we connect the Micro USB as power supply on the breadboard and provide VCC and ground voltages required. Then we assemble the clock cycle.

We use 555 IC, Resistors, capacitors, connecting wires.

The 555 timer IC is used to generate a clock signal which controls the timing and sequence of the random number generation process.

Resistors are used to limit the current flow and set specific voltage levels, while capacitors are used to store and release electrical energy.

We then check whether clock cycle is working properly using oscilloscope. If it forms a square wave it is working properly.

Then we assemble the remaining circuit for random number generation using Seven Segment Display, Decoder, Flip Flop, X-OR GATE.

The seven-segment display is used to display the generated random numbers. It consists of seven in-

dividual segments that make different combinations to represent digits from 0 to 9.



Decoder takes a binary-coded decimal input and decodes it to drive the appropriate segments of the seven-segment display.

The flip-flops store a single binary bit of information and are used to generate and store the random sequences of binary digits.

The X-OR gate helps introduce randomness and unpredictability into the generated binary sequences.

We assemble the XOR gate then flipflops then the Decoder connect them all using wires then connect the decoder to the Seven Segment Display. We then also connect the clock cycle to the assembly.

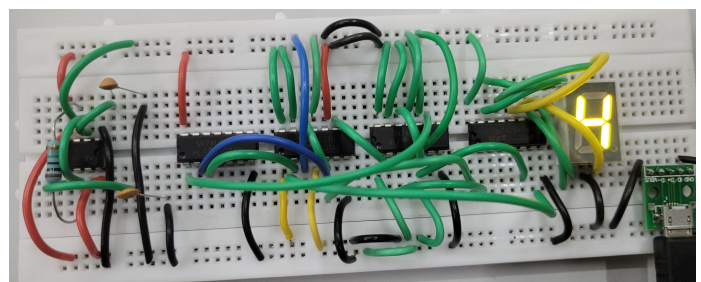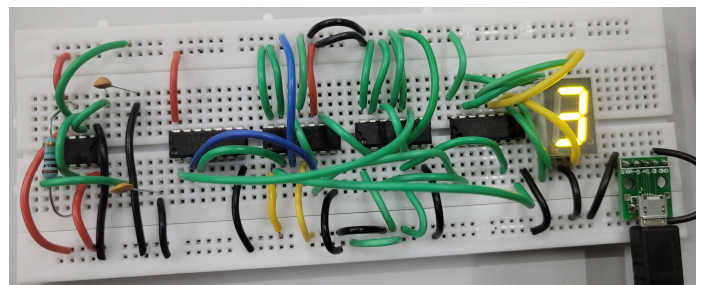Now we can see random numbers generating by connecting the Micro USB to the power source.



Observation: The produced binary numbers were converted and displayed on a 7-segment display. The 555 timer-based random clock introduced variations

and unpredictability in the clock signal, resulting in random numbers generated by circuit.

